

**Conventional Paper-I-2013**

- 1.(a) (i) What are ferroelectric materials ? What advantages do they have over conventional dielectric materials?
- (ii) Give one example each of a dielectric and a ferroelectric material having high relative permittivity ( $\epsilon_r$ ).
- (b) P-n junction transistors can be fabricated using the materials Germanium and Silicon. However silicon is preferred to Germanium. Explain.
- (c) Find the power spectral density if autocorrelation function is given as:  
 $R_x(\tau) = e^{-\alpha|\tau|}$  for  $-\infty < \tau < \infty$ .
- (d) Find  $v_1$  and  $v_2$  by writing a single supernode equation for the given circuit.

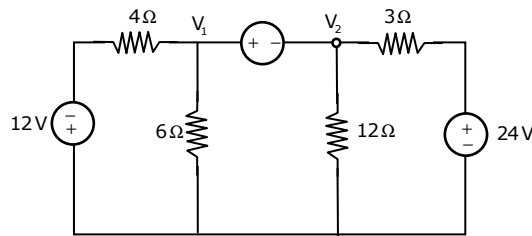


Figure: Q.1(d)

- (e) Two concentric spherical shells ( $r_1 = 5\text{cm}$  and  $r_2 = 30\text{cm}$ ) are applied with  $-10\text{ V}$  and  $+120\text{ V}$  respectively. The dielectric medium between the shells has  $\epsilon_r = 2.2$ . Find the charge densities. Determine the location where the  $V=50\text{V}$ .
- (f) Three signals (0.1 GHz, 1 GHz and 10 GHz) are available for propagation. Will it be possible to send all of them through a parallel plate air filled waveguide with a separation of 12 cm between the plates?
- (g) In an oscilloscope X- and Y-signals both are saw-tooth waves of same amplitudes and time periods but different phase angles. If Y-input is leading the X-input by  $90^\circ$ , draw the pattern traced on the CRO screen. Take the saw-tooth signals with positive slopes.
- (h) (a) Explain in brief the working of the circuit shown when  
 (i) The switch  $S_1$  is ON  
 (ii) The switch  $S_1$  is OFF.
- (b) What will be the output  $V_o$  when  $V_i$  is  $5\sin 100\pi t$  and

- (i)  $S_1$  is OFF  $\begin{cases} S_2 \text{ ON} \\ S_2 \text{ OFF} \end{cases}$
- (ii)  $S_1$  is ON  $\begin{cases} S_2 \text{ ON} \\ S_2 \text{ OFF} \end{cases}$

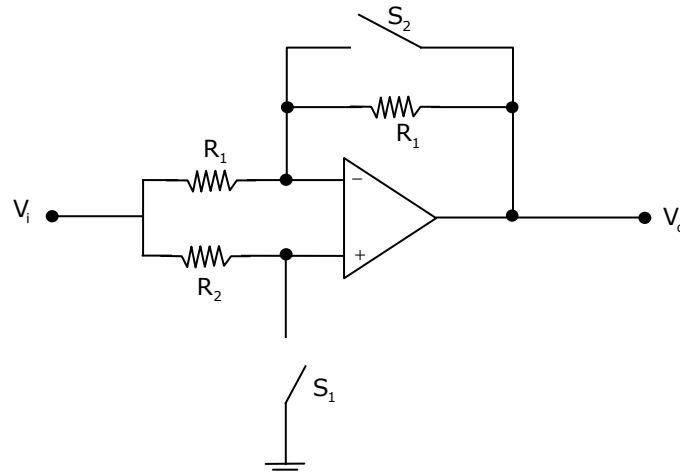


Figure: Q.1(h)

2. (a) What are the expressions for series and parallel resonances of the equivalent circuit of a quartz crystal oscillator ?
- (b) A quartz crystal oscillator has an equivalent inductance of  $L = 10\text{mH}$  and series and parallel capacitances of  $C_s = 10\mu\text{F}$  and  $C_p = 10\mu\text{F}$ . Find the series and parallel resonant frequencies of this oscillator.
- (c) Show schematically the static characteristics of a thyristor identifying clearly various regions.
- (d) What is a direct band gap and an indirect band gap semiconductor?
- (e) Explain why a silicon diode cannot be used as a LED but it is useful as a photodiode?
- (f) If Si diode is used as a photodiode find the maximum value of responsivity and maximum wavelength up to which it can be used.
- (g) A magnetically levitated train travels between the city centre and the airport in Shanghai, China. Which peculiar property of super-conductivity is taken advantage of in this application?

3. (a) A Zener diode regulates at 50 V over a range of diode currents from 5 mA to 40 mA. Supply voltage  $V = 200V$ .
- (i) Calculate the value of  $R$  to allow voltage regulation from a load current  $I_L = 0$  upto  $I_{max}$ , the maximum possible value of  $I_L$ .
- (ii) What is  $I_{max}$  ?
- (b) A half wave rectifier having a diode with an internal resistance of  $20\Omega$  is to supply power to a  $1k\Omega$  load from a  $110 V$  (rms) source of supply.

**Do the following:**

- (a) Draw a schematic that represents the above description of the circuit.

**Also calculate:**

- (b) Peak load current  
 (c) DC load current  
 (d) AC load current  
 (e) DC diode voltage.

- (c) Find the circuit shown, neglecting base currents find  $I_0$  and  $I_1, I_2, I_3$ .

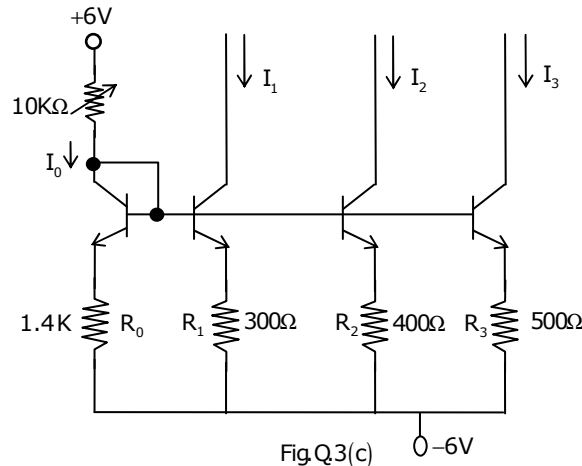


Fig.Q.3(c)

- (d) In the following circuit:

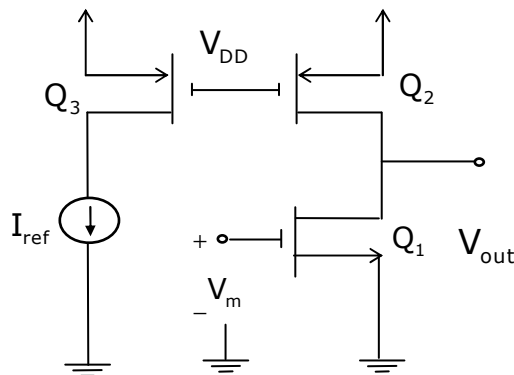


Figure: Q.3 (d)

If  $V_{DD} = 10V$ ,  $V_{tn} = |V_{tp}| = 1V$ ,  $\mu_n C_{ox} = 2\mu_p C_{ox} = 20\mu A / v^2$ ,  $W = 100 \mu m$ ,  $L = 10\mu m$  and  $|V_A| = \text{Early voltage} = 100V$  both for n and p devices,  $I_{ref} = 100 \mu A$ , find the small signal voltage gain.

4. (a) Find the energy  $E_x$  of the signal  $x(t) = e^{-at} u(t)$ . Determine the frequency  $W$  (rad/sec) so that the energy contributed by the spectral components of all frequencies below  $W$  is 95% of the signal energy.
- (b) Given that  $X(w)$  is the Fourier transform of  $x(t)$ . Find the Fourier transform of following in terms of  $X(w)$ :
- (i)  $x_1(t) = x(1-t) + x(-1-t)$
- (ii)  $x_2(t) = x(4t-5)$
- (iii)  $x_3(t) = \frac{d^2x}{dt^2}(t-1)$
- (c) The output  $y(t)$  of a continuous time LTI system is found to be  $3e^{-4t} u(t)$  when the input  $x(t)$  is  $u(t)$ .
- (i) Find the impulse response  $h(t)$  of the system.
- (ii) Find the output  $y(t)$  when the input  $x(t)$  is  $e^{-t}u(t)$ .
- (d) Consider the discrete time system as shown in the figure below:

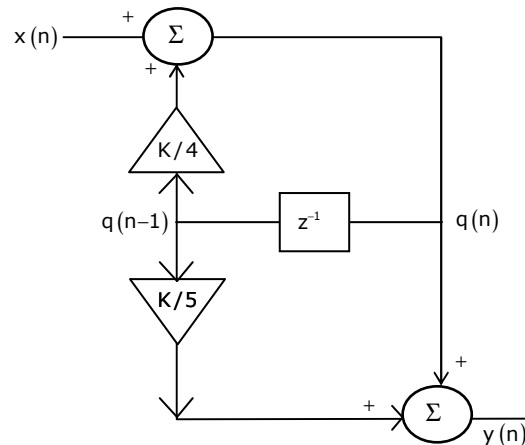


Figure: Q.4 (d)

For what value of  $K$  is the system BIBO stable.

5. (a) State and prove maximum power transfer theorem for a circuit with source  $V_s$  and source resistance  $R_s$  and a variable load resistance  $R_L$ .

- (b) If  $R_L$  is fixed and  $R_s$  is varied will the formula be valid? Prove.
- (c) For the circuit shown determine  $Z_L$  that will draw maximum power from the source.

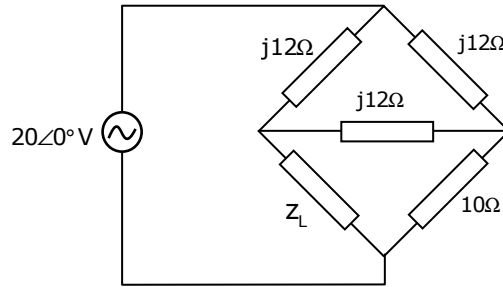


Figure: Q.5(c)

- (d) Determine the h-parameters of the network shown.

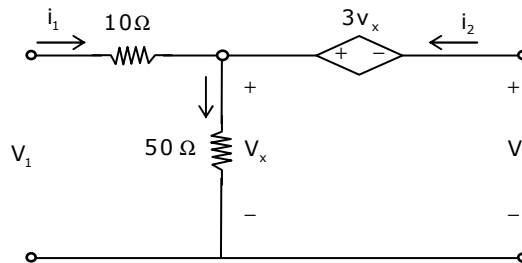


Figure: Q.5 (d)

6. (a) A pair of isolated parallel power lines of 1 cm radius with a separation of 90 cm have a voltage difference of 440 V. These power lines are 60 cm above a pair of telephone lines. Find the voltage difference between the telephone lines due to induction from power lines. The telephone lines are separated by 20 cm.
- (b) Two coils kept on a common axis are separated by 12 cm. Coil A has 10 turns of radius 4 cm with a current of 1 A. Coil B has 5 turns of wire with a radius of 6 cm. The current in Coil B is to be determined such that the induced magnetic field due to this current cancels the magnetic field at the center of Coil A generated by Coil A.

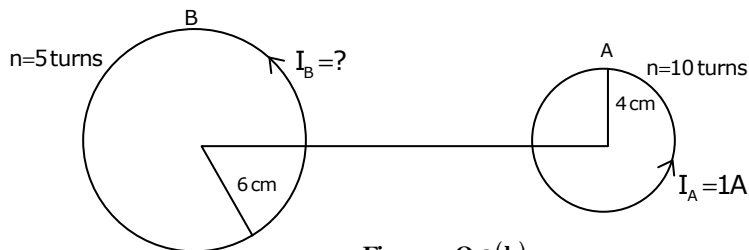


Figure: Q.6(b)

- (c) Derive the expression for the power required to move a current carrying conductor at a rotational frequency of  $N$  rev/min if it is placed in a magnetic field of flux density  $B_0 \hat{a}_r$ . Find the value with the given data.  $B_0 = 0.6\text{T}$ ;  $I = 10\text{A}$ ;  $L = 1.2\text{m}$ ;  $N = 25$  rev / min,  $r = 2\text{cm}$ . From this determine the magnetic flux density to be applied if the power is to be  $1.5\text{W}$ .

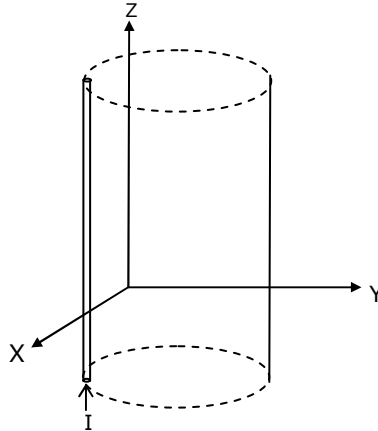


Figure: Q.6 (C)

- (d) A plane wave travelling in the  $+z$  direction in free space ( $z < 0$ ) is normally incident at  $z = 0$  on a conductor ( $z > 0$ ) for which  $\sigma = 61.7\text{MS/m}$ ,  $\mu_r = 1$ . The free space wave has a frequency of  $2.5\text{MHz}$ . The  $\vec{E}$  field amplitude is  $1.5\text{V/m}$  at the interface. Find the expression for  $\vec{H}$  in the conductor.

7. (a) In the circuit shown,  $R$  is a resistive transducer. The bridge is balanced and the output,  $V_o = 0$  when  $R_3 = R$ . Now  $R$  is changing in response to a physical variable. Show

$$\text{that the output voltage } V_o = V_R \left( 1 + \frac{R_2}{R_1} \right) \frac{\Delta R}{2R + \Delta R}$$


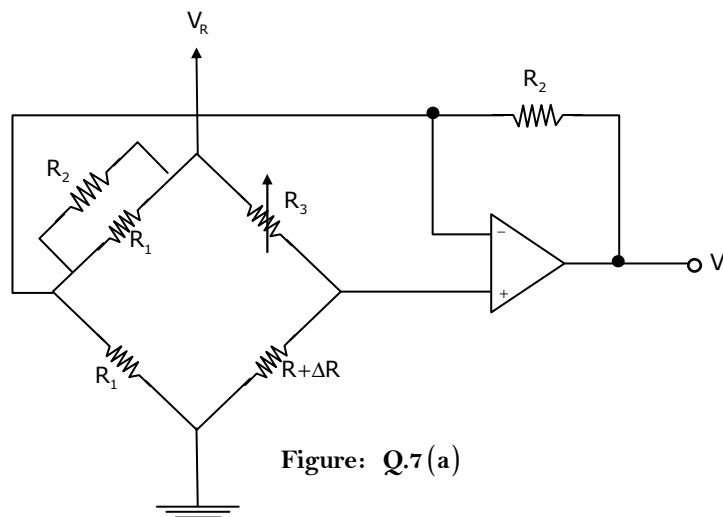


Figure: Q.7(a)

where  $\Delta R$  is the change in the value of  $R$ .

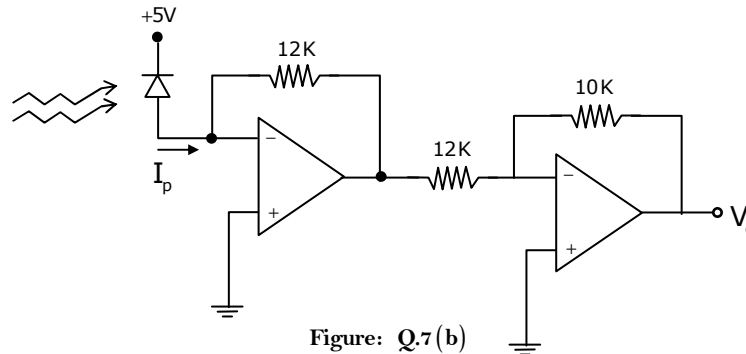- (b) In the circuit shown, the output voltage is found to be 25 mV. If the optical power input is at a wavelength,  $\lambda = 1.32\mu\text{m}$ . Calculate the optical power in  $\mu\text{W}$ . Take the quantum efficiency of the photo-diode to be 65%.



- (c) Overall quantum efficiency of GaAs light emitting diode shown in the circuit is 70%. ON state diode voltage is 1.8 V.  $V_i$  is a binary signal with  $V(1) = 5\text{V}$  and  $V(0) = 0\text{V}$ . Find the logic levels of the optical binary output. Take band-gap energy for GaAs = 1.43 eV.

