

Total number of printed pages – 7

B. Tech

CPES 5203

Fourth Semester Examination – 2009

DIGITAL ELECTRONICS CIRCUITS

Full Marks – 70

Time : 3 Hours

Answer Question No. 1 which is compulsory
and any **five** from the rest.

The figures in the right-hand margin
indicate marks.

1. Answer the following questions : 2×10
- (a) Binary number system is used in digital electronics circuits. Why octal, decimal or hexadecimal number systems are not used in circuit levels ?
 - (b) What will be the correct answer during subtraction of unsigned numbers using

P.T.O.

1's complement method for the following ?
Mention whether the answer is a positive number or a negative number.

- (i) end-carry occurs
 - (ii) end-carry does not occur
- (c) Convert the following function to "product of sums".
- $$F = A'B'C + AB'C' + AB'C + ABC' + ABC$$
- (d) What is "Prime Implicant" ? When it is said to be essential ?
- (e) "Pair" is a group of two logical 1's in a Karnaugh map. A "pair" eliminates one variable in the product term. Justify how one variable is eliminated ?
- (f) Are "NOR-OR" and "OR-NAND" functions equivalent ? justify.
- (g) Why both "S" and "R" inputs or a S-R latch should never be "1" simultaneously ?

(h) What will happen if the frequency of the clock signal connected to a flip-flop is increased to a very high value or decrease to a very low value ?

(i) Distinguish the functions of Decoder, Encoder and Multiplexer circuits.

(j) Draw the logic diagram of the digital circuit specified by the following hardware description language.

```
module circ (A, B, C, D, F) ;
```

```
input A, B, C, D ;
```

```
output F;
```

```
wire w, x, y, z, a, d ;
```

```
and (x, B, C, d) ;
```

```
and (y, a, C)
```

```
and (w, z, B)
```

```
or (z, y, A) ;
```

```
or (F, x, w) ;
```

```
not (a, A) ;
```

```
not (d, D)
```

```
endmodule
```

2. (a) In a tabular form, write the "2421" code and "Excess-3" code of decimal digit "0 to 9". What are the special properties of these codes ? 4

(b) Prove the following Boolean theorems using Huntington postulates without using the truth table and the principle of duality.

(i) $x + x = x$ and $x \cdot x = x$

(ii) $x + 1 = 1$ and $x \cdot 0 = 0$ 6

3. (a) Express the Boolean function as a sum-of-min terms. 5

$$F = A + B'C$$

Now, convert the sum-of-min terms to another canonical form.

(b) Simplify the following Boolean function and draw a circuit to represent the function

$$F(w, x, y, z) = \sum 0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14$$

4. (a) Implement the following function. 5

$$F = A(CD+B) + BC' \text{ using NAND gates.}$$

$$F = (A+B)(C+D)E \text{ using NOR gates.}$$

(b) Draw the circuit diagram of a 2 bit by 2 bit binary multiplexer using half-adder and logic gates. Explain its operation. 5

5. (a) Design a combinational circuit that converts a 4-bit Gray code to a 4-bit binary number. Implement the circuit using Exclusive-OR gates. 5

(b) A sequential circuit has two JK flip-flops A and B, and one input x. The circuit is described by the following flip-flop input equations.

$$J_A = x \quad K_A = B'$$

$$J_B = x \quad K_B = A$$

Derive the state equations of $A(t+1)$ and $B(t+1)$. Also draw the state diagram of the circuit. 5

6. (a) Design a sequential circuit with two D flip-flops A and B , and one input x . When $x = 0$, the state of the circuit remains the same. When $x = 1$, the circuit goes through the state transitions from 00 to 01 to 11 to 10 back to 00 and repeats. 5
- (b) Design a 4-bit binary synchronous counter with D flip-flops. 5
7. (a) How many $32\text{K} \times 8$ RAM chips are needed to provide a memory capacity of 256 K bytes? How many lines of the address must be used to access 256 K bytes? How many of these lines are connected to the address inputs of all chips? How many lines must be decoded for the chip select input? Specify the size of the decoder. 5

(b) Describe in brief the construction, circuit diagrams and operations of MOS and CMOS logic circuits. 5

8. Write a brief note on any *two* : 5+5

(a) ASCII code

(b) Magnitude Comparator

(c) Modulo-10 Counter

(d) ROM: