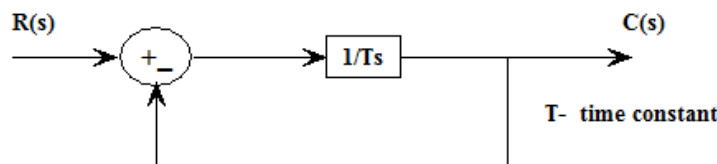

	INDIAN SPACE RESEARCH ORGANISATION	SET A
	ELECTRICAL	

1. For the system to be stable, in a negative feedback systems, with increase of feedback loops the range of gain (K)
- Reduces
 - Increases
 - Does not change
 - Exponentially increases

2. What is the impulse response for the system indicated below?




- $\frac{1}{T} e^{-\frac{t}{T}} u(t)$
 - $T e^{-Tt} u(t)$
 - $\frac{1}{T} e^{-\frac{t}{T}}$
 - $T e^{-Tt}$
3. The open loop transfer function of a unity feedback control system is $G(s) = \frac{K}{(s+2)(s+1)(s^2+6s+25)}$. Determine the range of gain ' K ' for the unity feedback control system to be stable.
- $+200 < K < 666.25$
 - $-200 < K < 112.17$
 - $-200 < K < 666.25$
 - $0 < K < 200$

	INDIAN SPACE RESEARCH ORGANISATION	SET A
	ELECTRICAL	

4. For the step response $C(s) = \frac{10(s-2)}{s(s^2+4s+5)}$ find initial and final value of $C(s)$.

- (a) Initial value = 0, Final value = 0
- (b) Initial value = 0, Final value = -4
- (c) Initial value = 0, Final value = cannot determine
- (d) Initial value = cannot determine, Final value = 0

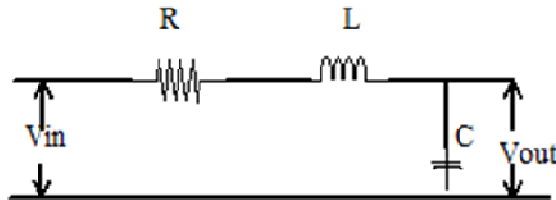5. What is the condition for the below system to be critically damped?



- (a) $R\sqrt{\frac{L}{C}} = 1$
- (b) $\frac{R}{2}\sqrt{\frac{L}{C}} = 1$
- (c) $\frac{1}{\sqrt{LC}} = 1$
- (d) $\frac{R}{2}\sqrt{\frac{C}{L}} = 1$

6. Transfer function of two compensators are:


$$C_1 = \frac{100(S+3)}{(S+200)} \quad C_2 = \frac{S+200}{100(S+3)}$$

Which of the following statement is correct?

- (a) C_1 - lead and C_2 - lag
- (b) C_1 - lag and C_2 - lead
- (c) Both C_1 and C_2 are lag
- (d) Both C_1 and C_2 are lead




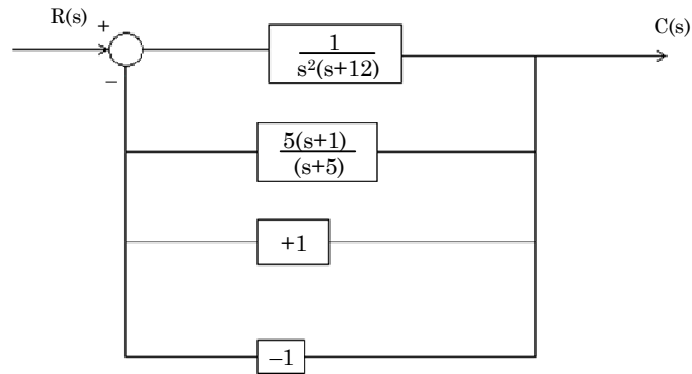7. In the system shown below, what is steady state error in unit ramp response?



- (a) 5/4
- (b) 4/5
- (c) 3/5
- (d) 5/5

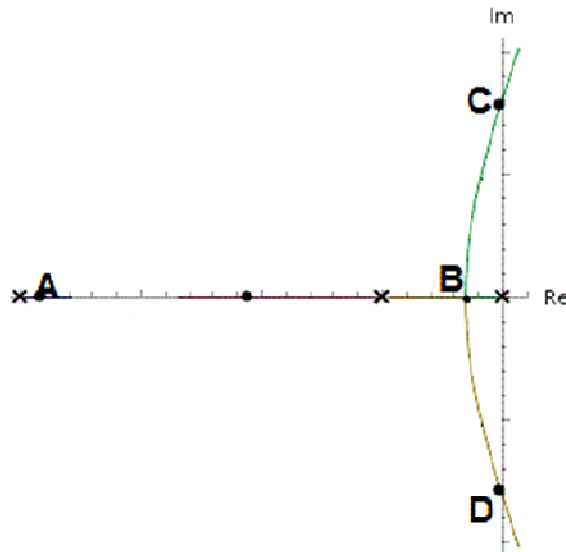
8. Typical root locus diagram of a system is shown below. Find the point where the system is critically damped.



- (a) At Point 'A'
- (b) At Point 'B'
- (c) At Points 'C' and 'D'
- (d) None of the above




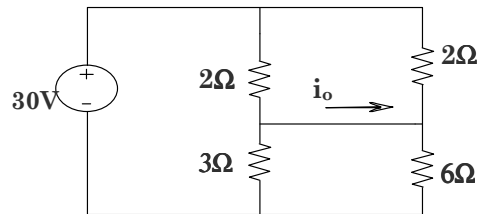12. Calculate i_o for the circuit diagram given below :




- (a) $5/3$ A
- (b) $-5/3$ A
- (c) $10/3$ A
- (d) $-10/3$ A

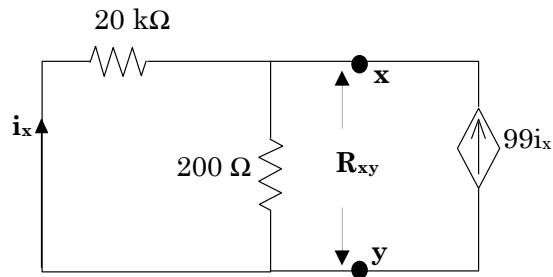13. In the circuit given below, calculate the value of R_{xy} .




- (a) 100Ω
- (b) 200Ω
- (c) 198.01Ω
- (d) $20 \text{ k}\Omega$

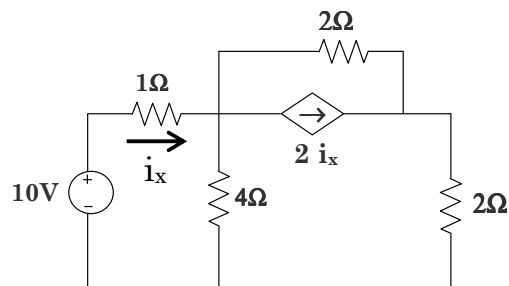14. Calculate i_x in the circuit diagram given below:



- (a) 2 A
- (b) 10 A
- (c) 5 A
- (d) None of the above

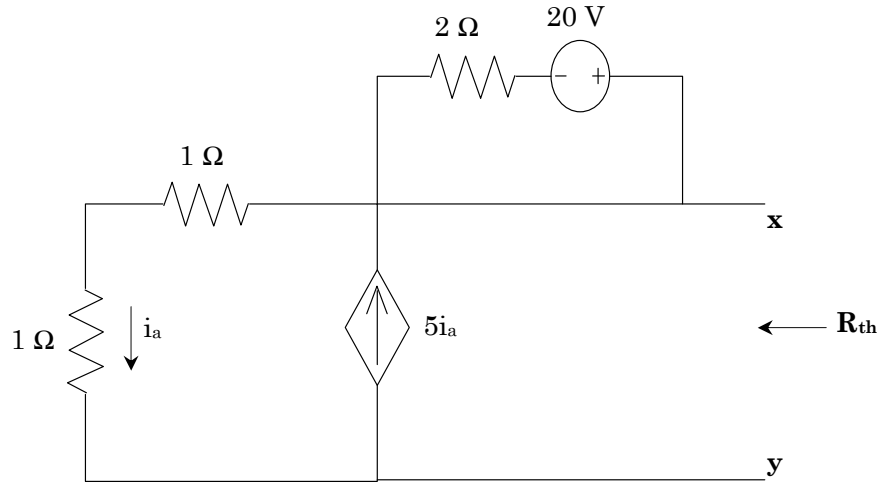
15. For the circuit given below, what is the value of Thevenin equivalent resistance (R_{th}) across the terminals x and y.



- | | |
|-------------------|-------------------|
| (a) $+1/2 \Omega$ | (b) $-1/2 \Omega$ |
| (c) 1Ω | (d) 2Ω |

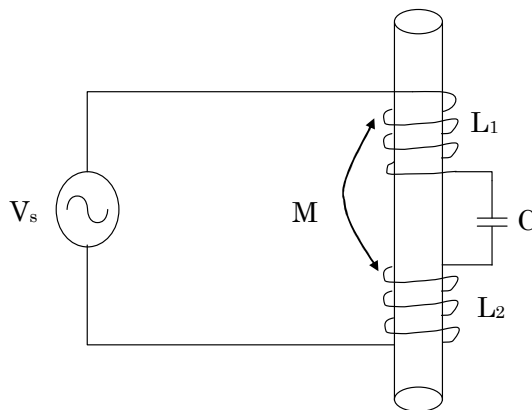
16. What is the resonant frequency of circuit shown below?

Where $R = 10 \Omega$, $L_1 = L_2 = 20 \text{ mH}$, Mutual Inductance $M = 5 \text{ mH}$, $C = 0.05 \mu\text{H}$.




- | | |
|--------------|--------------|
| (a) 4.18 kHz | (b) 2.88 kHz |
| (c) 5.18 kHz | (d) 3.18 kHz |

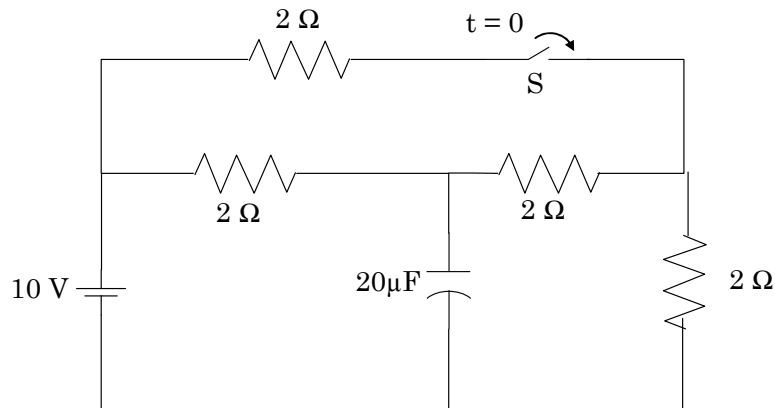17. What is the time constant of the circuit shown below, when $t = 0$ the Switch S is closed?




- (a) 26.67 μ Sec (b) 80 μ Sec
(c) 16 μ Sec (d) 24 μ Sec

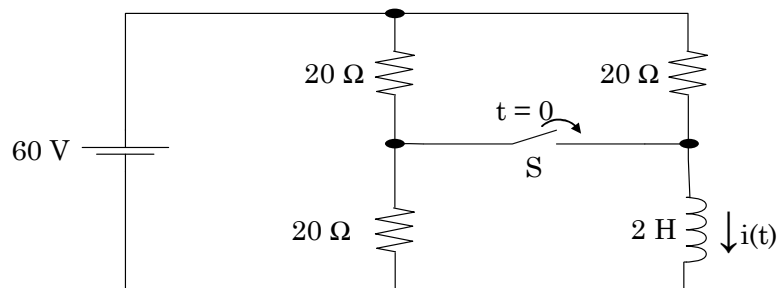18. At time $t = 0$ Switch S is closed in the circuit shown. What is the expression for the current $i(t)$ through the inductor?




- (a) $6 - (3 \times e^{-10t})$ (b) $6 - (3 \times e^{-10t/3})$
(c) $6 - (3 \times e^{-5t})$ (d) $6 - (3 \times e^{-5t/3})$

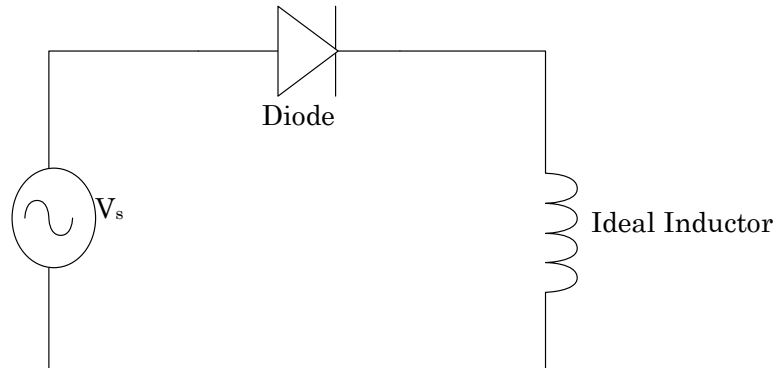
22. In the circuit given below Inductor used is ideal inductor, What is the conduction angle of diode?




- (a) 90° (b) 180°
(c) 270° (d) 360°
23. A single phase full bridge converter supplies power to constant current load. If the triggering angle is 45° , what is the input power factor of the converter?
- (a) 0.637
(b) 0.837
(c) 0.937
(d) None of the above
24. Input voltage $v = 230 \sin(100\pi t)$ Volts is given to a converter and the current drawn by the converter is $i = 20 \sin\left(100\pi t - \frac{\pi}{3}\right) + 10 \sin(300\pi t + 45^\circ) + 2 \sin\left(700\pi t - \frac{\pi}{6}\right)$ Amps. What is the active power drawn by the converter?
- (a) 2300 W (b) 1150 W
(c) 4324 W (d) 2162 W

	INDIAN SPACE RESEARCH ORGANISATION	SET A
	ELECTRICAL	

25. If a boost converter operates with a duty ratio $D = 1$ then output voltage is
- Infinity
 - Input voltage
 - Zero
 - Two times the input voltage
26. In a single phase asymmetrical half controlled rectifier with firing angle ' α ' feeds a constant current load. What will be conduction angle of diodes?
- $\pi + \alpha$
 - $\pi - \alpha$
 - 2α
 - 2π
27. In a three phase half controlled rectifier with constant current load and freewheeling diode, what is the fraction of cycle the diode conducts? Consider firing angle (α) of thyristors greater than 60° .
- $(\alpha - \pi/3)/2\pi$
 - $(\alpha + \pi/3)/2\pi$
 - $(\alpha - \pi/3) \times 3/2\pi$
 - $(\alpha + \pi/3) \times 3/2\pi$
28. A step down chopper operates from a D.C. voltage source $V_s = 400$ V and feeds a DC motor armature with a back emf $E_b = 300$ V. From the oscilloscope traces it is found that the current rises for a time $t_r = 10$ m sec and falls to zero over time $t_f = 5$ m sec and remains zero for a time of $t_o = 6$ m sec in every chopping cycle. Then, average DC voltage across the freewheeling diode will be
- 276 V
 - 257 V
 - 262 V
 - 300 V

	INDIAN SPACE RESEARCH ORGANISATION	SET A
	ELECTRICAL	

36. Two mechanically coupled alternators deliver power at 50 Hz and 60 Hz respectively. What is the highest speed of the alternators?
- (a) 3600 rpm (b) 3000 rpm
(c) 600 rpm (d) 500 rpm
37. A 3 Phase, 11 kV, 5 MVA alternator has synchronous reactance of 10Ω per phase. Its excitation is such that the generated emf is 14 kV. If the alternator is connected to infinite bus the maximum output of the alternator at a given excitation is
- (a) 15400 kW (b) 8000 kW
(c) 6200 kW (d) 5135 kW
38. The resultant flux density in the air gap of synchronous generator is lowest during:
- (a) Open Circuit (b) Solid Short Circuit
(c) Full Load (d) Half Load
39. A voltmeter gives 120 oscillations per minute when connected to the rotor of an induction motor. When the stator frequency is 50 Hz, what is the slip of the motor?
- (a) 2% (b) 2.5%
(c) 4% (d) 5%
40. A 6 pole, 3 phase alternator running at 1000 rpm supplies power to an 8 pole, 3 phase, induction motor which has a rotor current of frequency 2 Hz. What is the speed at which the motor operates?
- (a) 1000 rpm (b) 960 rpm
(c) 750 rpm (d) 720 rpm

	INDIAN SPACE RESEARCH ORGANISATION	SET A
	ELECTRICAL	


44. Impedance of single phase, two winding transformer referred to primary side is $0.1 + j 0.6$ p.u. The rating of the transformer is 200 V/400 V, 1 kVA. The per unit impedance is calculated on transformer base, then what is the equivalent impedance of transformer referred to secondary in ohms?

- (a) $80 + j 400 \Omega$ (b) $5 + j 25 \Omega$
(c) $16 + j 80 \Omega$ (d) None of the above

45. What is the order of sequence of impedance in salient pole alternator?


- (a) $Z_1 > Z_2 > Z_0$ (b) $Z_1 < Z_2 < Z_0$
(c) $Z_0 > Z_1 > Z_2$ (d) None of the above

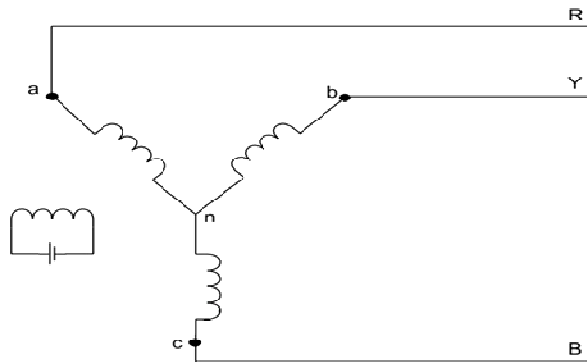46. A schematic diagram of an alternator is shown below where $V_{an} = V_{bn} = V_{cn} = V_1$.




If a single phase to ground fault occurs at location 'a', what will be the voltage at 'b' and 'c'?

- (a) $V_{bn} = V_{cn} = \sqrt{3} V_1$ (b) $V_{bn} = V_{cn} = V_1$
(c) $V_{bn} = V_{cn} = 0$ (d) None of the above

	INDIAN SPACE RESEARCH ORGANISATION	SET A
	ELECTRICAL	

51. Two buses in a system are maintained at the voltages $V_1 = 1.25 \angle 30^\circ$ and $V_2 = 1.35 \angle 25^\circ$. Bus 1 and Bus 2 are interconnected by a transmission line of impedance $(1.3 + j 7) \Omega$. The power flow direction is
- Real power flows from Bus 1 to Bus 2
 - Real power flows from Bus 2 to Bus 1
 - No real power flows between the buses
 - Reactive power flows from Bus 2 to Bus 1
52. Inductance of transmission line for a length of 400 kms in unsymmetrical configuration are:
 $L_R = 30 \text{ mH}$ $L_Y = 20 \text{ mH}$ $L_B = 25 \text{ mH}$
- What will be the inductance of each transmission line after transposing?
- $L_R = L_Y = L_B = 30 \text{ mH}$
 - $L_R = L_Y = L_B = 20 \text{ mH}$
 - $L_R = L_Y = L_B = 25 \text{ mH}$
 - $L_R = L_Y = L_B = 75 \text{ mH}$
53. A short transmission line is having series impedance $Z = 0.07 + j 0.12 \text{ p.u.}$. If the transmission line is operating under full load at leading p.f, what will be the possible voltage regulation of transmission line?
- 17%
 - 5%
 - 9%
 - 12%

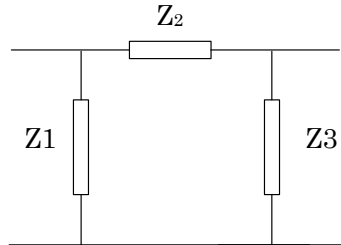54. Three networks are connected in cascade as shown below:




$A B C D$ parameters of the system is:


$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 2.0 \angle -10^\circ & 5 \angle 30^\circ \\ 1.0 \angle -20^\circ & 4.0 \angle 10^\circ \end{bmatrix}$$

What is the value of Z_2 ?


- | | |
|---------------------------|-------------------------|
| (a) $5 \angle 30^\circ$ | (b) $2 \angle 10^\circ$ |
| (c) $0.2 \angle 20^\circ$ | (d) $1 \angle 20^\circ$ |
55. The surge impedance of 400 km long overhead transmission line is 300 Ω . For a 200 km length of the same transmission line surge impedance will be
- | | |
|------------------|------------------|
| (a) 150 Ω | (b) 600 Ω |
| (c) 300 Ω | (d) 75 Ω |
56. In a power network, 380 kV is recorded at a 400 kV bus. A 60 MVAR, 400 kV shunt reactor is connected to the bus. What is the reactive power absorbed by the shunt reactor?
- | | |
|----------------|----------------|
| (a) 57 MVAR | (b) 54.15 MVAR |
| (c) 66.48 MVAR | (d) 63.16 MVAR |

	INDIAN SPACE RESEARCH ORGANISATION	SET A
	ELECTRICAL	


62. A Mod-6 counter is realized using 3 Nos. of flip-flops. The counter will skip
- (a) 4 Counts
(b) 3 Counts
(c) 2 Counts
(d) Zero Counts
63. An amplifier with negative feedback has overall gain of 100. The percentage change in gain with feedback and without feedback is 3% and 18% respectively. What is the feedback factor?
- (a) 0.05 (b) 0.02
(c) 0.04 (d) 0.10
64. Two voltmeters with ranges of 0 to 100 V has sensitivities as 10 k Ω /V and 20 k Ω /V. What is the maximum voltage that can be measured when these voltmeters are connected in series?
- (a) 200 V
(b) 150 V
(c) 100 V
(d) None of the above
65. An ammeter with range 0 to 2 mA has internal resistance of 10 Ω . What is the value of shunt resistance in order to increase the range of ammeter to 100 A?
- (a) 200 $\mu\Omega$ (b) 200 m Ω
(c) 2 $\mu\Omega$ (d) 2000 m Ω

	INDIAN SPACE RESEARCH ORGANISATION	SET A
	ELECTRICAL	


66. In a Dynamometer type wattmeter if current coil and voltage coil connections are interchanged then
- Current coil will damage
 - Voltage coil will damage
 - No damage
 - None of the above
67. In a linear system, an input of $5\sin\omega t$ produces an output of $10\cos\omega t$. The output corresponding to input $10\cos\omega t$ will be equal to:
- $+5\sin\omega t$
 - $-5\sin\omega t$
 - $+20\sin\omega t$
 - $-20\sin\omega t$
68. In an induction motor r_2' is the rotor resistance. What is the resistance representing mechanical output in the equivalent circuit of an induction motor as referred to stator side?
- $r_2' \left(\frac{1}{s} - 1 \right)$
 - $r_2'^2 / s$
 - $r_2'^2 \left(\frac{1}{s} - 1 \right)$
 - r_2' / s


	INDIAN SPACE RESEARCH ORGANISATION	SET A
	ELECTRICAL	

69. The pressure coil of a dynamometer type wattmeter is
- Highly inductive
 - Highly resistive
 - Purely resistive
 - Purely inductive
70. What is the octal equivalent of Hexadecimal number CD.AB?
- 320.506
 - 215.546
 - 205.516
 - 315.526
71. The present age of father is twice that of the elder son. 10 years later the age of the father will be three times that of the younger son. If the difference of ages of the two sons is 15 years, the age of father is
- 50 years
 - 100 years
 - 70 years
 - 60 years
72. The volume of a cone is equal to that of a cylinder whose height is 9 cm and diameter 60 cm. find the radius of the base of cone if its height is 108 cm.
- 12 cm
 - 18 cm
 - 10 cm
 - 15 cm

	INDIAN SPACE RESEARCH ORGANISATION	SET A
	ELECTRICAL	

77. Matrix A has following eigen values $\lambda_1 = +3j$, $\lambda_2 = +5j$, $\lambda_3 = +1j$, then the matrix is
- Symmetric matrix
 - Skew Hermitian matrix
 - Orthogonal matrix
 - None of the above
78. In a school, 45% of the students play football, 30% of students play cricket and 15% of students play both. If a student is selected at random what is the probability that he plays football or cricket?
- 1/4
 - 2/7
 - 3/5
 - 4/5
79. The maximum value of function $(xy)^6$ on the ellipse $\frac{x^2}{4} + y^2 = 1$ occur at a point (x, y) for which y^2 is equal to
- $\sqrt{2}/3$
 - 1/2
 - 2/3
 - 5/11
80. $y = \tan^{-1}(x^2/2)$ what is $\frac{dy}{dx}$?
- $4x/(4+x)$
 - $4/(4+x^2)$
 - $x/(4+x^2)$
 - $4x/(4+x^2)$

 इसरो isro	INDIAN SPACE RESEARCH ORGANISATION	SET A
	ELECTRICAL	

 इसरो isro	INDIAN SPACE RESEARCH ORGANISATION	SET A
	ELECTRICAL	