



- 13.(a)(i) Using small signal equivalent circuit determine the voltage gain and current gain of a Common emitter amplifier. (8)
- (ii) Using high frequency small signal model derive unity gain frequency of common emitter amplifier. (8)

OR

- 13.(b)(i) Using small signal equivalent circuit, determine the voltage gain and output resistance of a common source amplifier. (8)
- (ii) Using high frequency small signal circuit model, derive the unity gain frequency of a common source amplifier. (8)

- 14.(a)(i) Explain the large signal operation of differential amplifier using BJT and derive its common mode voltage gain. (8)
- (ii) Derive the small signal differential gain of the differential amplifier using BJT. (8)

OR

- 14.(b)(i) Explain the principle of operation of a single tuned amplifier with LC tank circuit. Derive the resonant frequency, gain at resonance and Q of the tuned amplifier. (16)

- 15.(a)(i) Give the advantages of negative feedback amplifier. (4)
- (ii) With a block diagram explain the various feedback topology of negative feedback Amplifier. (12)

OR

- 15.(b)(i) Explain the principle of operation of Wein-bridge oscillator and derive an expression for its resonant frequency (8)
- (ii) Explain the principle of operation of Hartley oscillator and derive its resonant frequency. (8)

-----